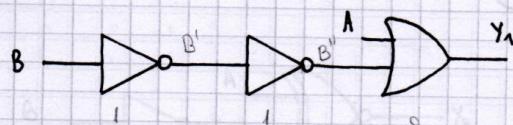


ROSATELLI, MARÍA FLORENCIA


①



HOJA N°


FECHA

A	B	Y_1
0	0	0
0	1	1
1	0	1
1	1	1

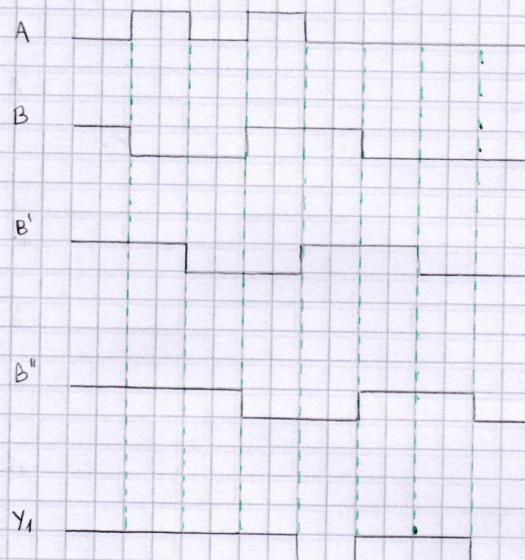


NOTA

ROSATELLI, MARIA FLORENIA

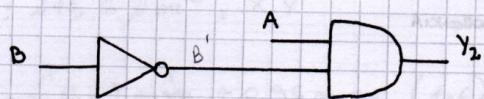

A	B	y_2
0	0	0
0	1	0
1	0	0
1	1	1

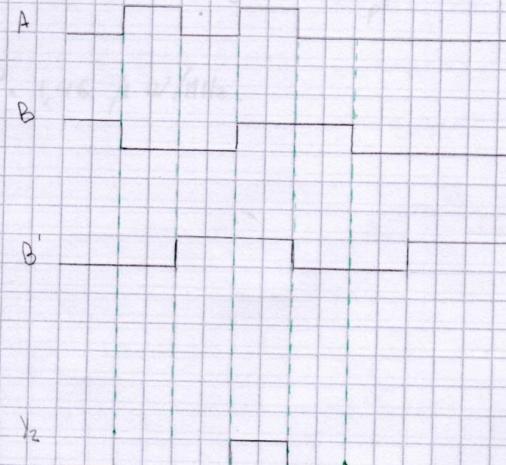


NOTA


ROSATELLI, MARÍA FloRENCIA

HOJA N°

FECHA

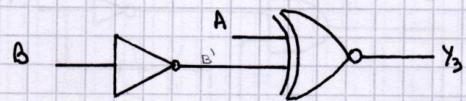


A	B	y_3
0	0	1
0	1	0
1	0	0
1	1	1

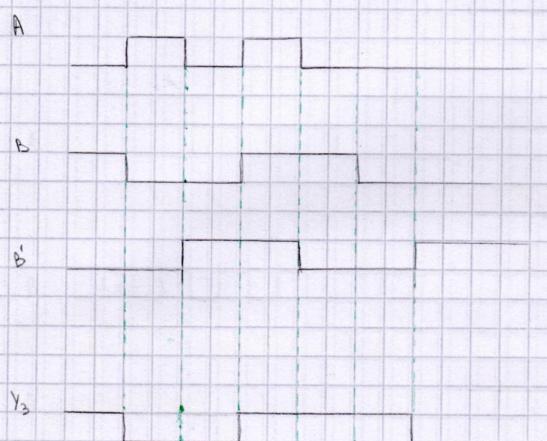







NOTA

ROSATELLI, MARÍA FLORENCIA

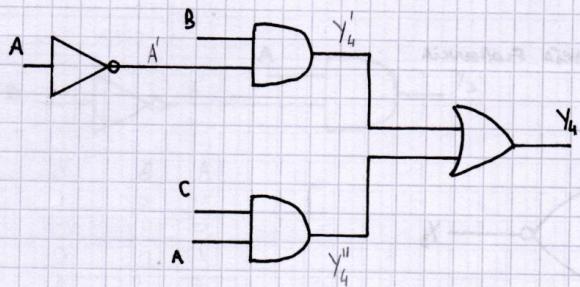

A'	A	B	Y_4'	A	C	Y_4
1	0	0	0	0	0	0
1	0	1	1	0	1	0
0	1	0	0	1	0	0
0	1	1	0	1	1	1

Y_4'	Y_4''	Y_4
0	0	0
0	1	1
1	0	1
1	1	1

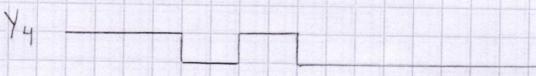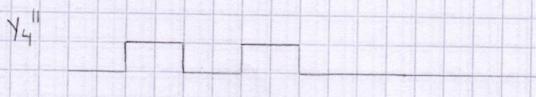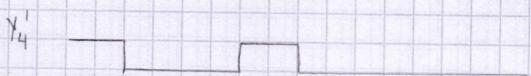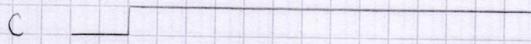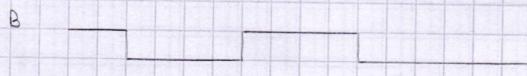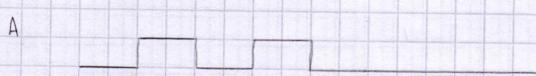


NOTA

ROSATELLI MARIA FLORENCIA


HOJA N°

FECHA - AÑO






①

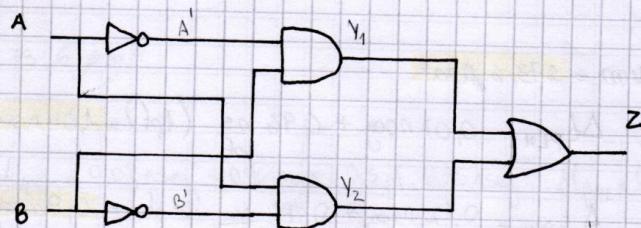

A	A'	B	Y ₁	A	B'	B	Y ₂
0	1	0	0	0	1	0	0
0	1	1	1	0	0	1	0
1	0	0	0	1	1	0	1
1	0	1	0	1	0	1	0

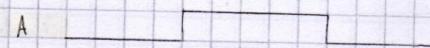

Y ₁	Y ₂	Z
0	0	0
0	1	1
1	0	1
1	1	1

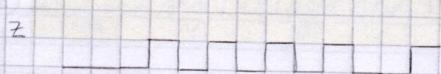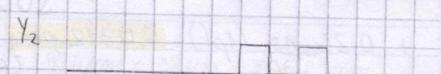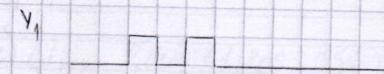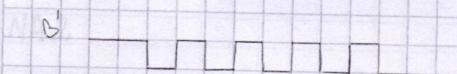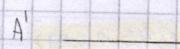

NOTA

③

ROSATELLI, MARÍA FLORENCIA

$$\text{CARGA} = 1 \text{ pF}$$

INV

$$\text{Área: } 7,2 \mu\text{m} \times 38,0 \mu\text{m} = 273,6 \mu\text{m}^2$$

$$\text{Tiempo de propagación: } \Delta t_{PLH} = 0,07 \text{ nseg} + 0,96 \frac{\text{ns}}{\text{pF}} (1 \text{ pF}) = 1,03 \text{ nseg}$$

$$\Delta t_{PHL} = 0,12 \text{ nseg} + 0,78 \frac{\text{ns}}{\text{pF}} (1 \text{ pF}) = 0,9 \text{ nseg}$$

$$\text{Consumo de potencia: } 1,46 \mu\text{W/MHz}$$

INV 2

$$\text{Área: } 7,2 \mu\text{m} \times 38 \mu\text{m} = 273,6 \mu\text{m}^2$$

$$\text{Tiempo de propagación: } \Delta t_{PLH} = 0,06 \frac{\text{nseg}}{\text{pF}} + 0,51 \frac{\text{ns}}{\text{pF}} (1 \text{ pF}) = 0,57 \text{ nseg.}$$

$$\Delta t_{PHL} = 0,10 \text{ nseg} + 0,35 \frac{\text{ns}}{\text{pF}} (1 \text{ pF}) = 0,45 \text{ nseg.}$$

$$\text{Consumo de potencia: } 2,31 \mu\text{W/MHz}$$

INV 3

$$\text{Área: } 13,4 \mu\text{m} \times 38 \mu\text{m} = 509,2 \mu\text{m}^2$$

$$\text{Tiempo de propagación: } \Delta t_{PLH} = 0,07 \frac{\text{ns}}{\text{pF}} + 0,28 \frac{\text{ns}}{\text{pF}} (1 \text{ pF}) = 0,35 \text{ nseg.}$$

$$\Delta t_{PHL} = 0,12 \text{ ns} + 0,26 \frac{\text{ns}}{\text{pF}} (1 \text{ pF}) = 0,312 \text{ nseg}$$

$$\text{Consumo de potencia: } 4,54 \mu\text{W/MHz}$$

NOTA

ROSATELLI, MARÍA FLORENCIA

HOJA N°

FECHA

④

INV

a) $273,6 \mu\text{m}^2$

b) 4

c) $\Delta t_{PLH} = 0,07 \text{nseg} + 0,96 \frac{\text{nseg}}{\text{pf}} \cdot 0,5 \text{pf} = 0,55 \text{nseg}$ $\Delta t_{PHL} = 0,12 \text{nseg} + 0,78 \frac{\text{nseg}}{\text{pf}} \cdot 0,5 \text{pf} = 0,51 \text{nseg}$

AN2

a) $509,2 \mu\text{m}^2$

b) 7

c) $\Delta t_{PLHA} = 0,69 \text{nseg}$, $\Delta t_{PLHB} = 0,75 \text{nseg}$ $\Delta t_{PHLA} = 0,81 \text{nseg}$, $\Delta t_{PHLB} = 0,79 \text{nseg}$

OR2

a) $13,8 \mu\text{m} \times 38 \mu\text{m} = 524 \mu\text{m}^2$

b) 6

c) $\Delta t_{PLHA} = 0,33 \text{ns} + 0,95 \frac{\text{ns}}{\text{pf}} \cdot 0,5 \text{pf} = 0,805 \text{ns}$ $\Delta t_{PHLA} = 0,33 \text{ns} + 0,78 \frac{\text{ns}}{\text{pf}} \cdot 0,5 \text{pf} = 0,71 \text{ns}$

NA2

a) $10 \mu\text{m} \times 38 \mu\text{m} = 380 \mu\text{m}^2$

b) 4

c) $\Delta t_{PLH} = 0,14 \text{ns} + 1,18 \frac{\text{ns}}{\text{pf}} \cdot 0,5 \text{pf} = 0,73 \text{ns}$ $\Delta t_{PHL} = 0,14 \text{nseg} + 0,97 \frac{\text{nseg}}{\text{pf}} \cdot 0,5 \text{pf} = 0,625 \text{nseg}$

N02

a) $9,6 \mu\text{m} \times 38 \mu\text{m} = 364,8 \mu\text{m}^2$

b) 4


c) $\Delta t_{PLHA} = 0,13 \text{nseg} + 1,83 \frac{\text{nseg}}{\text{pf}} \cdot 0,5 \text{pf} = 1,04 \text{nseg}$ $\Delta t_{PHLA} = 0,18 \text{nseg} + 1,02 \frac{\text{nseg}}{\text{pf}} \cdot 0,5 \text{pf} = 0,69 \text{nseg}$

$\Delta t_{PLHB} = 0,12 \text{nseg} + 1,83 \frac{\text{nseg}}{\text{pf}} \cdot 0,5 \text{pf} = 1,03 \text{nseg}$

NOTA

(5)

ROSATELLI, MARÍA FLORENCIA

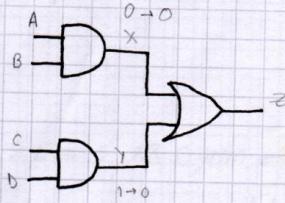


A	B	C	D	Z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	1	1	1	1

$$\text{Área} = (X_{\text{AND}} * Y_{\text{AND}}) + (X_{\text{AND}} * Y_{\text{AND}}) + (X_{\text{OR}} * Y_{\text{OR}}) = (13,8 \mu\text{m} * 38 \mu\text{m}) * 2 + (13,4 \mu\text{m} * 38 \mu\text{m}) \\ \Rightarrow \underline{\underline{1,55 \mu\text{m}^2}}$$

$$T = \Delta t_{\text{PLH(AND)}} + \Delta t_{\text{PLH(OR)}} = 0,81 \text{ nseg} + 0,69 \text{ nseg} = \underline{\underline{1,5 \text{ nseg}}} = \Delta t_{\text{LH}}$$

$$\Delta t_{\text{PLH(AND)}} + \Delta t_{\text{PLH(OR)}} = 0,75 \text{ nseg} + 0,805 \text{ nseg} = \underline{\underline{1,555 \text{ nseg}}} = \Delta t_{\text{LH}}$$
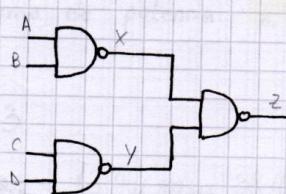
$$\text{Potencia} = 2 * P_{\text{AND}} + P_{\text{OR}} = 2 * (4,26 \mu\text{W/MHz}) + 4,16 \mu\text{W/MHz} = \underline{\underline{12,68 \mu\text{W/MHz}}}$$



A	B	C	D	Z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	1	1	1	1

$$\text{Área} = (X_{\text{NAND}} * Y_{\text{NAND}}) * 3 = (380 \mu\text{m}^2) * 3 = \underline{\underline{1,14 \mu\text{m}^2}}$$

$$T = 2 * \Delta t_{\text{PLH(NAND)}} = 2 * 0,73 \text{ nseg} = \underline{\underline{1,46 \text{ nseg}}} = \Delta t_{\text{LH}}$$

$$2 * \Delta t_{\text{PHL(NAND)}} = 0,62 \text{ nseg} * 2 = \underline{\underline{1,25 \text{ nseg}}} = \Delta t_{\text{HL}}$$

$$\text{Potencia} = 3 * P_{\text{NAND}} = 2,21 \mu\text{W/MHz} * 3 = \underline{\underline{6,63 \mu\text{W/MHz}}}$$

NOTA

NOTA	ROSATELLI, MARÍA FLORENCIA	HOJA N°
		FECHA

⑥


$A = 2 * (X_{op} * Y_{op}) + (X_{and} * Y_{and}) = 2 * (13,8 \mu m * 38 \mu m) + (13,4 \mu m * 33 \mu m) =$
 $\Rightarrow 1,55 \mu m^2$

$T = \Delta t_{PHL(op)} + \Delta t_{PHL(and)} = 0,805 \text{ nseg} + 0,75 \text{ nseg} = \underline{\underline{1,555 \text{ nseg}}}$

$\Delta t_{PHL(op)} + \Delta t_{PHL(and)} = 0,71 \text{ nseg} + 0,81 \text{ nseg} = \underline{\underline{1,52 \text{ nseg}}}$

Potencia = $4,26 \frac{\mu W}{MHz} + 2 * \left(4,16 \frac{\mu W}{MHz} \right) = \underline{\underline{12,58 \frac{\mu W}{MHz}}}$

ROSATELLI, MARÍA FLORENCIA

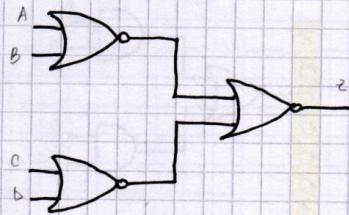

A	B	C	D	Z
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$\text{Área} = 3 * \text{NAND} = 3 * (9,6 \mu\text{m} * 38 \mu\text{m}) = 10,36 \text{ } \mu\text{m}^2$$

$$T = 2 * \Delta t_{PHL} = 2 * 1,04 \text{ nseg} = 2,08 \text{ nseg}$$

$$2 * \Delta t_{PHL} = 2 * 0,69 \text{ nseg} = 1,38 \text{ nseg}$$

$$\text{Potencia} = 3 * P_{non} = 3 * 2,21 \frac{\mu\text{W}}{\text{MHz}} = 6,63 \frac{\mu\text{W}}{\text{MHz}}$$

Dependiendo lo que se busca en optimización convierte uno o el otro circuito.

Por menos área, potencia, costo y Δt_{PHL} \rightarrow 2º circuito (NOR)

Por menor Δt_{PHL} \rightarrow 1º circuito (OR-AND)

NOTA


ROSATOU, MARÍA FLORENCIA

HOJA N°

FECHA

7)

selector	A	B	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

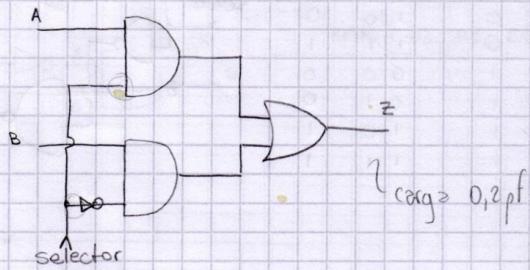

$$\text{Área} = 2 * (X_{\text{AND}} * Y_{\text{AND}}) + (X_{\text{(NOT)}} * Y_{\text{(NOT)}}) + (X_{\text{(OR)}} * Y_{\text{OR}}) = 2 * (509,2 \mu\text{m}^2) + (273,6 \mu\text{m}^2) + (524 \mu\text{m}^2)$$

$$\Rightarrow \underline{\underline{1,81 \mu\text{m}^2}}$$

$$\text{Nº transistores} = 2 * 7 + 4 + 6 = \underline{\underline{24}}$$

$$\Delta T \rightarrow$$

$$10\% C_{(\text{AND})} = 0,1 \cdot (0,033 \text{ pF}) = 0,0033 \text{ pF}$$

$$10\% C_{(\text{NOT})} = 0,1 \cdot (0,058 \text{ pF}) = 0,0058 \text{ pF}$$

$$10\% C_{(\text{OR})} = 0,1 \cdot (0,036 \text{ pF}) = 0,0036 \text{ pF}$$

$$\rightarrow \Delta t_{px} = t_{pt} + \Delta t_{pe} \left(C_{fanin} \cdot 0,1 + C_{fanout} (\text{compuerta siguiente}) \right) \Bigg|_{\text{NOT + AND + OR}}$$

$$\rightarrow 0,12 \text{ ns} + 0,96 \frac{\text{ns}}{\text{pF}} (0,0058 \text{ pF} + 0,033 \text{ pF}) + 0,4 \text{ ns} + 0,82 \frac{\text{ns}}{\text{pF}} (0,0033 \text{ pF} + 0,036 \text{ pF}) +$$

$$+ 0,35 \text{ ns} + 0,95 \frac{\text{ns}}{\text{pF}} (0,0036 \text{ pF} + 0,2 \text{ pF}) = 0,157 \text{ ns}_{\text{seg}} + 0,432 \text{ ns}_{\text{seg}} + 0,543 \text{ ns}_{\text{seg}} =$$


$$\underline{\underline{1,133 \text{ ns}_{\text{seg}}}}$$

NOTA

b)

selector	A	B	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

notas de maría florencia

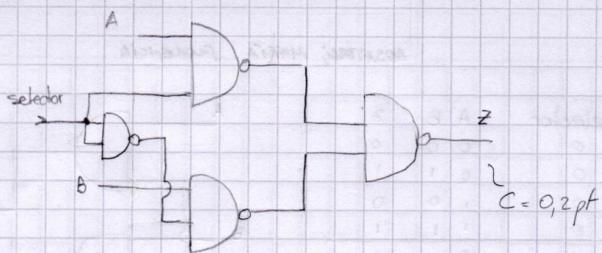

$$\text{Área} = 4 (X_{(\text{NAND})} * Y_{(\text{NAND})}) = 4 (380 \text{ nm}^2) = 1,52 \text{ nm}^2$$

$$\text{Nº de transistores} = 4 * 4 = 16$$

$$\Delta T \rightarrow$$


$$C_{(\text{NAND})} = 0,1 \cdot (0,050 \text{ pF}) = 0,0050 \text{ pF}$$

$$\Delta t_{\text{pxx}} = 2 \left[\frac{0,14 \text{ nseg}}{\text{pf}} + 1,18 \text{ ns} (0,0050 \text{ pF} + 0,05 \text{ pF}) \right] + \frac{0,14 \text{ nseg} + 1,18 \text{ ns}}{\text{pf}} (0,0050 \text{ pF} + 0,2 \text{ pF})$$

$$\Rightarrow 0,41 \text{ nseg} + 0,382 \text{ nseg} \approx 0,792 \text{ nseg}$$

Para los círculos de Z, considero los peores casos de retraso entre A y B y entre el low-high, high-low.

NOTA

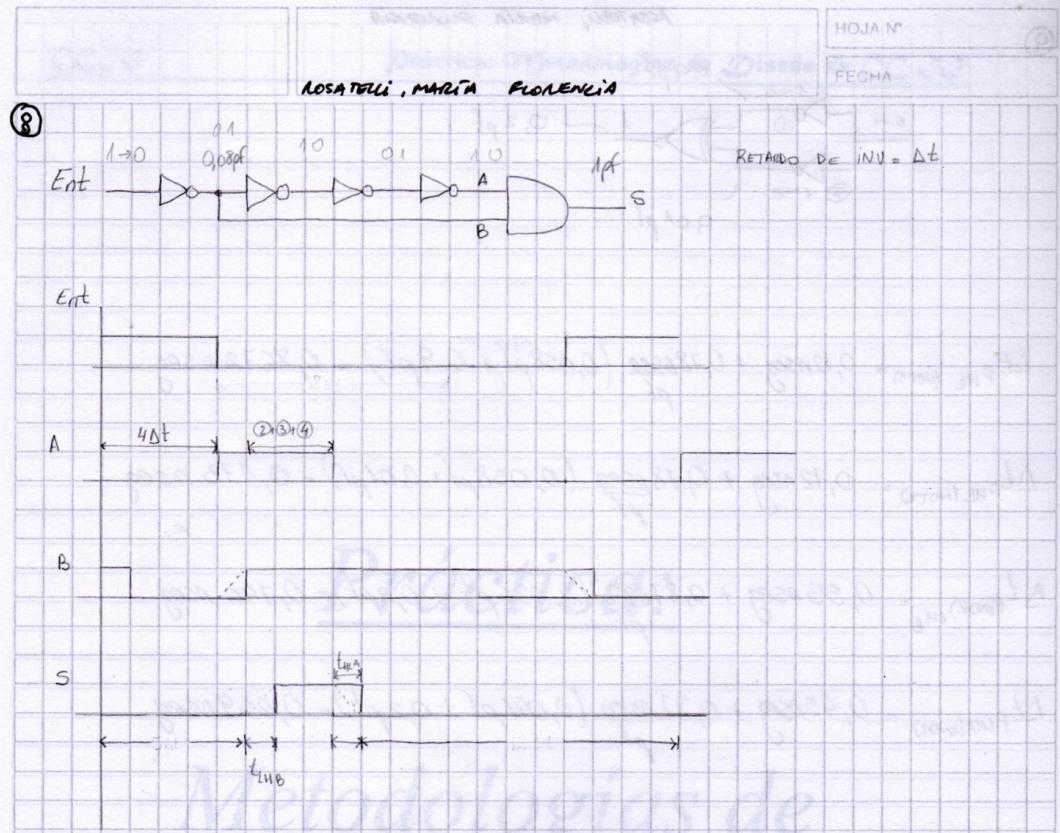

$$1) \Delta t_{PLH} = 0,07 \text{nseg} + 0,96 \text{nseg} (0,08 \text{pf} + 0,058 \text{pf} + 0,033 \text{pf}) = 0,234 \text{nseg}$$

$$2) \Delta t_{PH} = 0,12 \text{nseg} + 0,78 \text{nseg} (0,08 \text{pf} + 0,058 \text{pf}) = 0,227 \text{nseg}$$

$$3) \Delta t_{PLH} = 0,07 \text{nseg} + 0,96 \text{nseg} (0,08 \text{pf} + 0,058 \text{pf}) = 0,202 \text{nseg}$$

$$4) \Delta t_{PHL} = 0,12 \text{nseg} + 0,78 \text{nseg} (0,08 \text{pf} + 0,029 \text{pf}) = 0,205 \text{nseg}$$

$$\Delta t_{PHLA} = 0,40 \text{nseg} + 0,82 \frac{\text{nseg}}{\text{pf}} (0,08 \text{pf} + 1 \text{pf}) = 1,2856 \text{nseg}$$

$$\Delta t_{PLHE} = 0,36 \text{nseg} + 0,78 \frac{\text{nseg}}{\text{pf}} (0,08 \text{pf} + 1 \text{pf}) = 1,2024 \text{nseg}$$

$$\Delta T = t_{LH_B} - ② - ③ - ④ = 1,2024 \text{nseg} - 0,227 \text{nseg} - 0,202 \text{nseg} - 0,205 \text{nseg} = 0,5684 \text{nseg}$$


$$\Rightarrow \Delta T + \Delta t_{PHLA} = 1,854 \text{nseg}$$

NOTA

ATOR

ROSATELLI, MARINA FLORENCIA

⑨

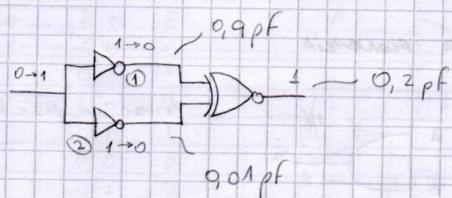


$$\Delta t_{PHL(NOT_1)} = 0,12 \text{ nseg} + \frac{0,78 \text{ nseg}}{\text{pf}} (0,058 \text{ pf} + 0,9 \text{ pf}) = 0,8672 \text{ nseg}$$

$$\Delta t_{PHL(NOT_2)} = 0,12 \text{ nseg} + \frac{0,78 \text{ nseg}}{\text{pf}} (0,058 \text{ pf} + 0,01 \text{ pf}) = 0,173 \text{ nseg}$$

$$\Delta t_{PLH(xnor)}_{LH_B} = 0,55 \text{ nseg} + \frac{0,87 \text{ nseg}}{\text{pf}} (0,026 \text{ pf} + 0,2 \text{ pf}) = 0,746 \text{ nseg}$$
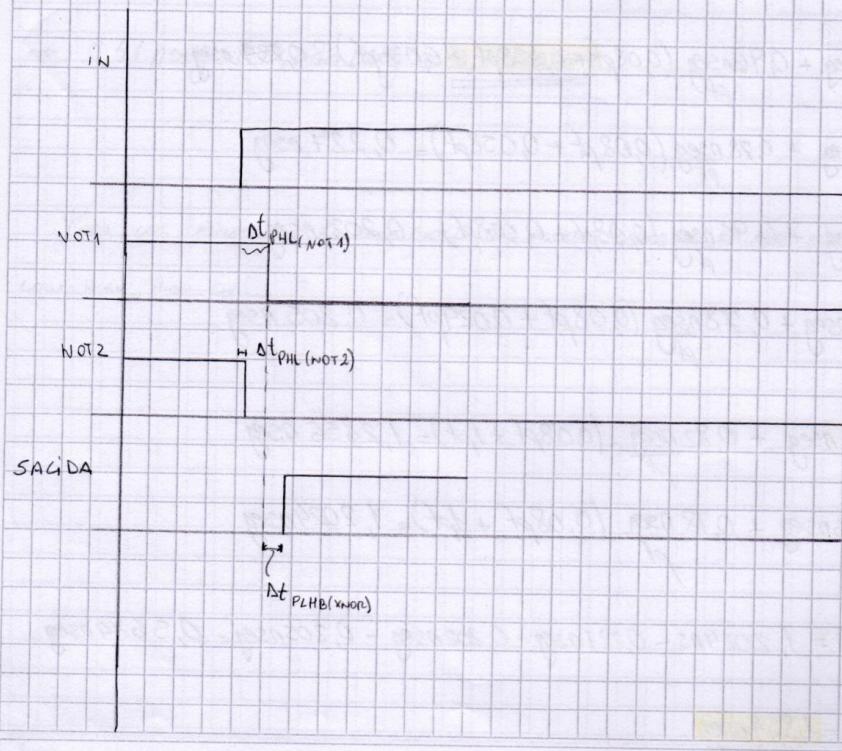
$$\Delta t_{PLH(xnor)} = 0,45 \text{ nseg} + \frac{0,87 \text{ nseg}}{\text{pf}} (0,041 \text{ pf} + 0,2 \text{ pf}) = 0,659 \text{ nseg}$$



NOTA

NOTA