

1)

a-(pego el Código desde otro ide porque, si no, no me entraba en la captura)

```
library ieee;
use ieee.std_logic_1164.all;

entity tabla_d_verdad is
port
    (a,b,cin: in std_logic;
    cout, s: out std_logic
    );
end tabla_d_verdad;

architecture estructura of tabla_d_verdad is
begin

process (a, b, cin)
begin

    if (std_logic_vector'(a, b, cin)="000") then
        (cout, s)<=std_logic_vector'("00");


    elsif ((std_logic_vector'(a, b, cin)="001") or (std_logic_vector'(a, b, cin)="010") or (std_logic_vector'(a, b, cin)="100")) then
        (cout, s)<=std_logic_vector'("01");

    elsif (std_logic_vector'(a, b, cin)="111") then
        (cout, s)<=std_logic_vector'("11");

    else (cout, s)<=std_logic_vector'("10");

    end if;
end process;

end estructura;
```

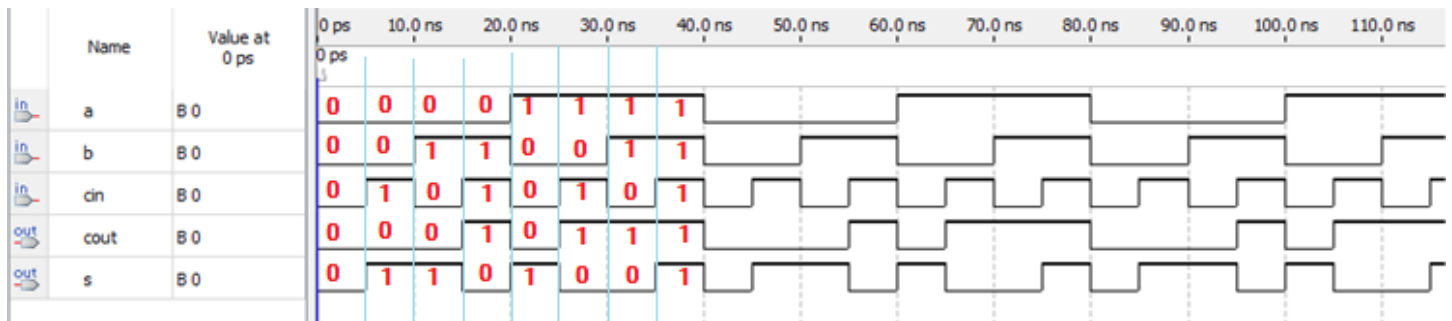

b-

```
library ieee;
use ieee.std_logic_1164.all;

entity Tabla_de_verdad_b is
port
    (a,b,cin: in std_logic;
    cout, s: out std_logic
    );
end Tabla_de_verdad_b;


architecture estructura of Tabla_de_verdad_b is
begin

process (a, b, cin)
begin

    case std_logic_vector'(a, b, cin) is
        when "000" => (cout, s)<=std_logic_vector'("00");
        when "001" | "010" | "100" => (cout, s)<=std_logic_vector'("01");
        when "111" => (cout, s)<=std_logic_vector'("11");
        when others => (cout, s)<=std_logic_vector'("10");

    end case;
end process;

end estructura;
```

 

c-

```

library ieee;
use ieee.std_logic_1164.all;


entity tabla_de_verdad_c is
port (a,b,cin: in std_logic;
      cout, s: out std_logic
      );
end tabla_de_verdad_c;

architecture estructura of tabla_de_verdad_c is
begin

    (cout, s)<=std_logic_vector("00") when std_logic_vector'(a, b, cin)="000" else
               std_logic_vector("01") when std_logic_vector'(a, b, cin)="001" else
               std_logic_vector("01") when std_logic_vector'(a, b, cin)="010" else
               std_logic_vector("01") when std_logic_vector'(a, b, cin)="100" else
               std_logic_vector("11") when std_logic_vector'(a, b, cin)="111" else
               std_logic_vector("10");

end estructura;

```

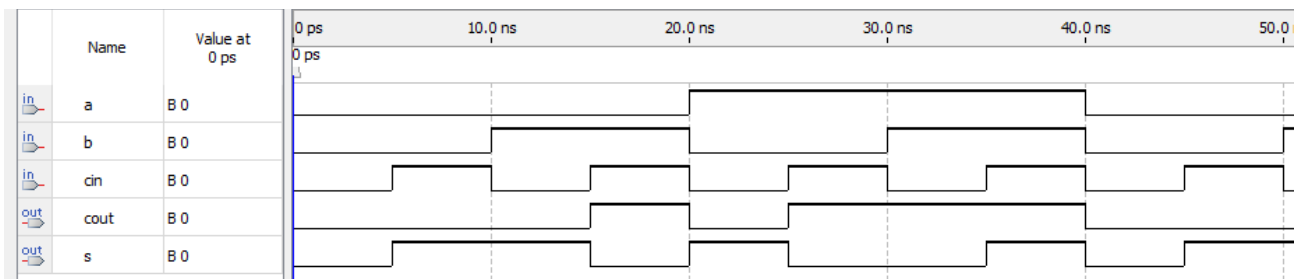

d-

```

library ieee;
use ieee.std_logic_1164.all;


entity tabla_de_verdad_d is
port (a,b,cin: in std_logic;
      cout, s: out std_logic
      );
end tabla_de_verdad_d;

architecture estructura of tabla_de_verdad_d is
begin

with std_logic_vector'(a, b, cin) select
    (cout, s)<=std_logic_vector'("00") when "000",
    std_logic_vector'("01") when "001",
    std_logic_vector'("11") when "111",
    std_logic_vector'("10") when others;

end estructura;

```

 

e-

```

library ieee;
use ieee.std_logic_1164.all;

package TablaDeVerdadPaquete is
    function Suma (a, b, cin: std_logic) return std_logic_vector;
end TablaDeVerdadPaquete;

package body TablaDeVerdadPaquete is
function Suma (a, b, cin: std_logic) return std_logic_vector is
    variable s: std_logic;
    variable cout: std_logic;
begin
    if (std_logic_vector'(a, b, cin)="000") then
        (cout, s):=std_logic_vector'("00");
    elsif ((std_logic_vector'(a, b, cin)="001") or (std_logic_vector'(a, b, cin)="010") or (std_logic_vector'(a, b, cin)="100")) then
        (cout, s):=std_logic_vector'("01");
    elsif (std_logic_vector'(a, b, cin)="111") then
        (cout, s):=std_logic_vector'("11");
    else (cout, s):=std_logic_vector'("10");
    end if;
    return (cout, s);
end Suma;
end TablaDeVerdadPaquete;

```

```

library ieee;
use ieee.std_logic_1164.all;


library work;
use work.TablaDeVerdadPaquete.all;

entity tabla_de_verdad_e is
port  (a,b,cin: in std_logic;
       cout, s: out std_logic
       );
end tabla_de_verdad_e;

architecture estructura of tabla_de_verdad_e is
begin
    (cout, s)<=std_logic_vector'(suma(a, b, cin));

end estructura;

```

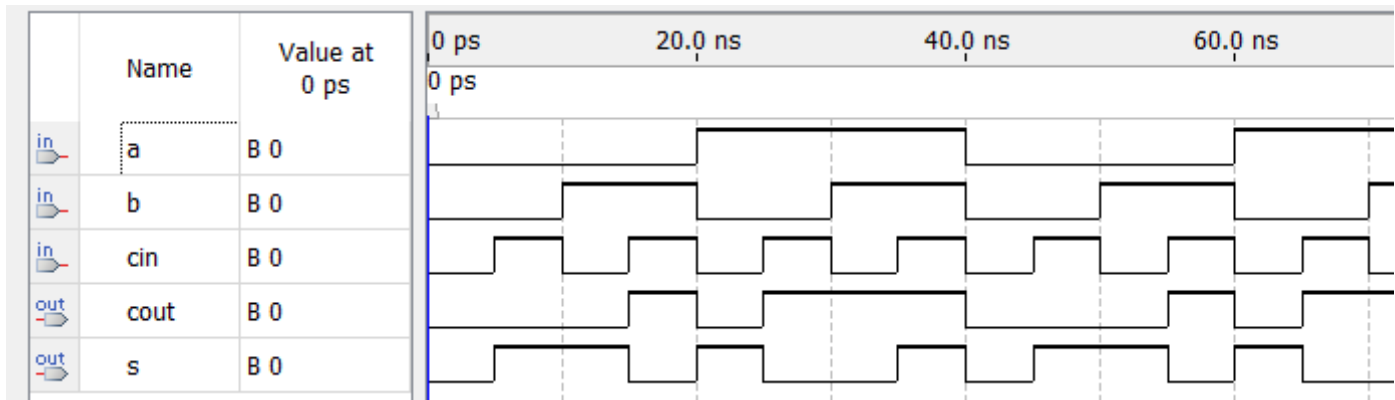

2)

```
use ieee.numeric_std.all;

entity tabla_de_verdad_2 is
port      (a: in std_logic_vector(11 downto 0);
           salida: out std_logic_vector(6 downto 0)
           );
end tabla_de_verdad_2;

architecture estructura of tabla_de_verdad_2 is
begin

process (a)
begin

    if std_match(a(11 downto 0), "0110110-----") then
        salida<=("1000100");

    elsif std_match(a(11 downto 0), "1110110-----") then
        salida<=("1001000");

    elsif std_match(a(11 downto 0), "-----010-----") then
        salida<=("0000001");

    elsif std_match(a(11 downto 0), "1100110-----") then
        salida<=("0100000");

    elsif std_match(a(11 downto 0), "0100110-----") then
        salida<=("0010000");

    elsif std_match(a(11 downto 0), "-1---10--111") then
        salida<=("0000001");

    elsif std_match(a(11 downto 0), "1---10--111") then
        salida<=("0000001");

    elsif std_match(a(11 downto 0), "-----100111-") then
        salida<=("0000010");


    elsif std_match(a(11 downto 0), "--1--10--111") then
        salida<=("0000001");

    elsif std_match(a(11 downto 0), "---1-10--111") then
        salida<=("0000001");

    else
        salida<=("1111111");
    end if;

end process;

end estructura;
```

 

3) a-


```

library ieee;
use ieee.std_logic_1164.all;

entity multiplexor is
port (a, b: in std_logic_vector(7 downto 0);
      sel: in std_logic;
      y: out std_logic_vector (7 downto 0)
);
end multiplexor;

architecture estructura of multiplexor is
begin
process (a, b, sel)
begin
    if (sel='1') then
        y<=b;
    elsif (sel='0') then
        y<=a;
    else
        y<="ZZZZZZZZ"|;
    end if;
end process;
end estructura;

```

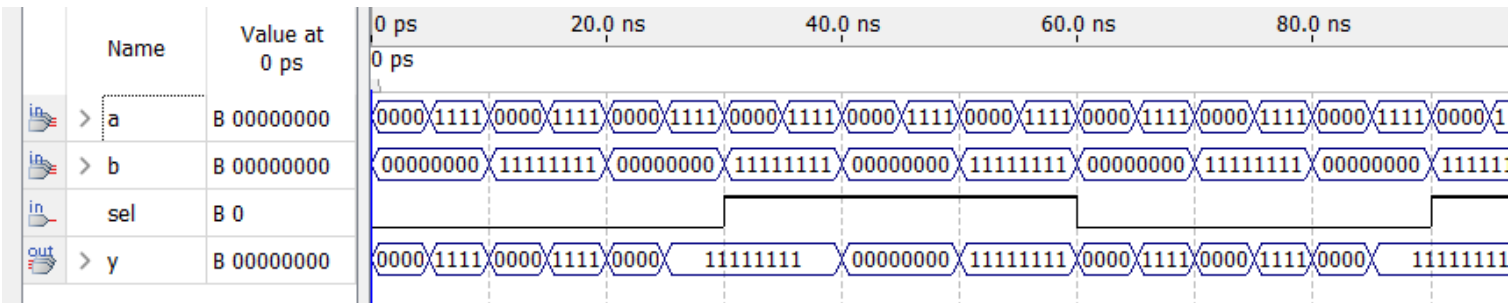

b-

```


library ieee;
use ieee.std_logic_1164.all;

entity multiplexor_b is
port  (a, b: in std_logic_vector(7 downto 0);
       sel: in std_logic;
       y: out std_logic_vector (7 downto 0)
       );
end multiplexor_b;

architecture estructura of multiplexor_b is
begin
process (a, b, sel)
begin
    case sel is
        when '1' => y<=b;
        when '0' => y<=a;
        when others => y<="ZZZZZZZZ";

    end case;
end process;
end estructura;

```

 

c-

```


library ieee;
use ieee.std_logic_1164.all;

entity multiplexor_c is
port  (a, b: in std_logic_vector(7 downto 0);
       sel: in std_logic;
       y: out std_logic_vector (7 downto 0)
       );
end multiplexor_c;

architecture estructura of multiplexor_c is
begin
    One: y<=a when sel='0' else
          b when sel='1' else
          "ZZZZZZZZ";

end estructura;

```

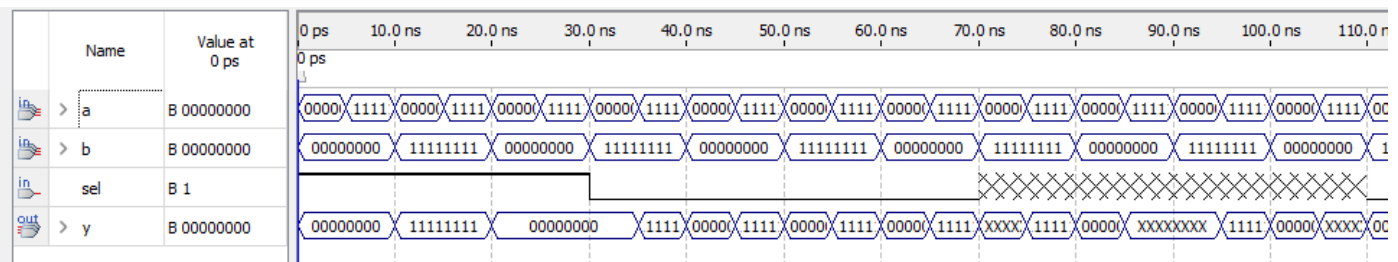

d-


```

library ieee;
use ieee.std_logic_1164.all;


entity multiplexor_d is
port (a, b: in std_logic_vector(7 downto 0);
      sel: in std_logic;
      y: out std_logic_vector(7 downto 0)
);
end multiplexor_d;

architecture estructura of multiplexor_d is
begin
    with sel select
        y<=a          when '0',
           b          when '1',
           "ZZZZZZZZ" when others;
end estructura;

```

 

4)

 

X	Y	Z	D0	D1	D2	D3	D4	D5	D6	D7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1


```

library ieee;
use ieee.std_logic_1164.all;

entity deco_a is
port (a: in std_logic_vector(2 downto 0);
      y: out std_logic_vector (7 downto 0)
      );
end deco_a;


architecture estructura of deco_a is
begin

    with a select
        y<=
            "00000001"      when "111",
            "00000010"      when "110",
            "00000100"      when "101",
            "00001000"      when "100",
            "00010000"      when "011",
            "00100000"      when "010",
            "01000000"      when "001",
            "10000000"      when "000",

            "ZZZZZZZZ"      when others;

end estructura;

```

 

b-

```

library ieee;
use ieee.std_logic_1164.all;

entity decodificador_b is
port (a: in std_logic_vector(2 downto 0);
      y: out std_logic_vector (7 downto 0)
      );
end decodificador_b;

architecture estructura of decodificador_b is
begin

    process (a)
    begin

        case a is

            when "000"=> y<="10000000";
            when "001"=> y<="01000000";
            when "010"=> y<="00100000";
            when "011"=> y<="00010000";
            when "100"=> y<="00001000";
            when "101"=> y<="00000100";
            when "110"=> y<="00000010";
            when "111"=> y<="00000001";


            when others => y<="ZZZZZZZZ";

        end case;

    end process;

end estructura;

```

 

C-

```

library ieee;
use ieee.std_logic_1164.all;


entity decodificador_c is
port (a: in std_logic_vector(2 downto 0);
      y: out std_logic_vector(7 downto 0)
);
end decodificador_c;

architecture estructura of decodificador_c is
begin
process (a)
    variable i: integer:=0;
begin
    for i in 0 to 7 loop
        case a is
            when "000"=> y<="10000000";
            when "001"=> y<="01000000";
            when "010"=> y<="00100000";
            when "011"=> y<="00010000";
            when "100"=> y<="00001000";
            when "101"=> y<="00000100";
            when "110"=> y<="00000010";
            when "111"=> y<="00000001";

            when others => y<="ZZZZZZZZ";

        end case;
    end loop;
end process;
end estructura;

```

 

5)

a-

```

library ieee;
use ieee.std_logic_1164.all;




entity codificador_a is
port (a: in std_logic_vector(7 downto 0);
      y: out std_logic_vector (2 downto 0)
      );
end codificador_a;


architecture estructura of codificador_a is
begin
    y<="000" when a = "10000000" else
        "001" when a = "01000000" else
        "010" when a = "00100000" else
        "011" when a = "00010000" else
        "100" when a = "00001000" else
        "101" when a = "00000100" else
        "110" when a = "00000010" else
        "111" when a = "00000001" else

        "ZZZ";

end estructura;

```

   

 

b-


```

library ieee;
use ieee.std_logic_1164.all;

entity codificador_b is
port (a: in std_logic_vector(7 downto 0);
      y: out std_logic_vector (2 downto 0)
);
end codificador_b;

architecture estructura of codificador_b is
begin
process (a)
begin
if a = "10000000" then
y<="111";
elseif a = "01000000" then
y<="110";
elseif a = "00100000" then
y<="101";
elseif a = "00010000" then
y<="100";
elseif a = "00001000" then
y<="011";
elseif a = "00000100" then
y<="010";
elseif a = "00000010" then
y<="001";
elseif a = "00000001" then
y<="000";
else y<="ZZZ";
end if;
end process;
end estructura;

```

 

C-

```

library ieee;
use ieee.std_logic_1164.all;

entity codificador_c is
port (a: in std_logic_vector(7 downto 0);
      y: out std_logic_vector(2 downto 0)
);
end codificador_c;

architecture estructura of codificador_c is
begin
process (a)
    variable i: integer:=0;
    begin
        for i in 0 to 7 loop
            case a is
                when "10000000"=> y<="000";
                when "01000000"=> y<="001";
                when "00100000"=> y<="010";
                when "00010000"=> y<="011";
                when "00001000"=> y<="100";
                when "00000100"=> y<="101";
                when "00000010"=> y<="110";
                when "00000001"=> y<="111";

                when others => y<="ZZZ";

            end case;
        end loop;
    end process;
end estructura;

```



6)

a-

```
library ieee;
use ieee.std_logic_1164.all;

entity contador_a is
```

```

]entity contador_a is
]port ( clk, reset1: in std_logic;
-      y: out std_logic_vector(3 downto 0)
-      );
-end contador_a;

architecture estructura of contador_a is
]begin

]process (clk)

-    variable i: integer:=0;

begin

-    if rising_edge(clk) then

-        case i is

-            when 0 => y<="0000";
-            when 1 => y<="0001";
-            when 2 => y<="0010";
-            when 3 => y<="0011";
-            when 4 => y<="0100";
-            when 5 => y<="0101";
-            when 6 => y<="0110";
-            when 7 => y<="0111";
-            when 8 => y<="1000";
-            when 9 => y<="1001";
-            when 10 => y<="1010";
-            when 11 => y<="1011";
-            when 12 => y<="1100";
-            when 13 => y<="1101";
-            when 14 => y<="1110";
-            when 15 => y<="1111";

-            when others => y<="ZZZZ";


-        end case;
-        i:=i+1;

-    end if;

-    if reset1 = '1' then
-        i:=0;
-    end if;

-end process;
-end estructura;

```

 

b-

```

library ieee;
use ieee.std_logic_1164.all;

entity contador_b is
port ( clk, reset1, CE, L: in std_logic;
      L_num: in integer;
      y: out std_logic_vector(3 downto 0)
      );
end contador_b;


architecture estructura of contador_b is
begin
process (CE, L)
variable i: integer:=0;
begin
if reset1 = '1' then
    i:=0;
elseif CE='1' then
    if rising_edge(clk) then
        if L='1' then
            i:=L_num;
        else
            i:=i+1;
        end if;
    end if;
    case i is
        when 0 => y<="0000";
        when 1 => y<="0001";
        when 2 => y<="0010";
        when 3 => y<="0011";
        when 4 => y<="0100";
        when 5 => y<="0101";
        when 6 => y<="0110";
        when 7 => y<="0111";
        when 8 => y<="1000";
        when 9 => y<="1001";
        when 10 => y<="1010";
        when 11 => y<="1011";
        when 12 => y<="1100";
        when 13 => y<="1101";
        when 14 => y<="1110";
        when 15 => y<="1111";
        when others => y<="ZZZZ";
    end case;
end if;
end process;
end estructura;

```

```

        when 15 => y<="1111";
        when others => y<="ZZZZ";
    end case;
end process;
end estructura;

```

 c-

7)

a-

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;

entity hdlc_a is
port (clk, reset, Din: in std_logic;
      F: out std_logic);
end hdlc_a;

architecture estructura of hdlc_a is
    type e is (eReset, Primer0, Primer1, Segundol, Tercer1, Cuartol, Quintol, Sextol, Inicio);
    signal estado:e;

begin
    process(clk, reset)
    begin
        if reset = '0' then
            estado<=eReset;
        elsif (rising_edge(clk)) then
            case estado is
                when eReset => if Din='0' then
                    estado<=Primer0;
                else
                    estado<=eReset;
                end if;

                when Primer0 => if Din='1' then
                    estado<=Primer1;
                else
                    estado<=Primer0;
                end if;

                when Primer1 => if Din='1' then
                    estado<=Segundol;
                else
                    estado<=Primer0;
                end if;

                when Segundol => if Din='1' then
                    estado<=Tercer1;
                else
                    estado<=Primer0;
                end if;

                when Tercer1 => if Din='1' then
                    estado<=Cuartol;
                else
                    estado<=Primer0;
                end if;

                when Cuartol => if Din='1' then
                    estado<=Quintol;
                else
                    estado<=Primer0;
                end if;

                when Quintol => if Din='1' then
                    estado<=Sextol;
                else
                    estado<=Primer0;
                end if;

                when Sextol => if Din='1' then
                    estado<=eReset;
                else
                    estado<=Inicio;
                end if;
            end case;
        end if;
    end process;
end estructura;

```

```

when Inicio => if Din='1' then
    estado<=eReset;
else
    estado<=Primer0;
end if;

end case;
end if;
end process;

process (estado)


begin

    if estado=Inicio then
        F<='1';
    else
        F<='0';
    end if;

end process;

end estructura;


```

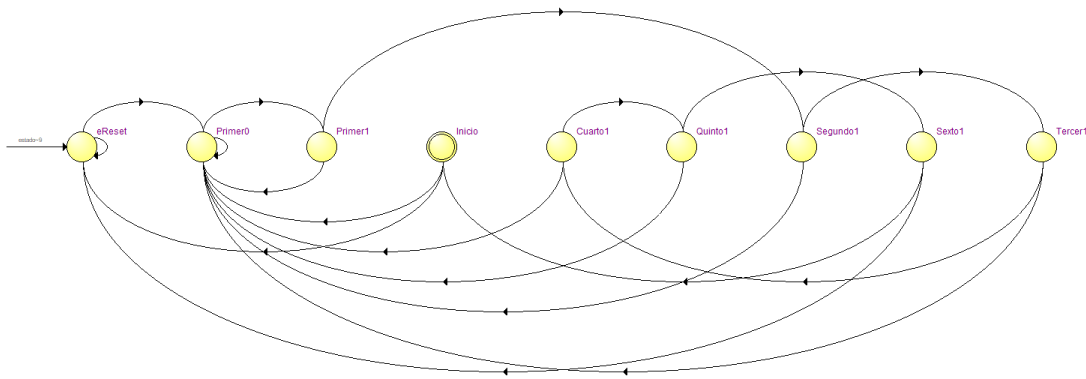

	Source State	Destination State	Condition
1	Cuarto1	Quinto1	(Din)
2	Cuarto1	Primer0	(!Din)
3	eReset	Primer0	(!Din)
4	eReset	eReset	(Din)
5	Inicio	Primer0	(!Din)
6	Inicio	eReset	(Din)
7	Primer0	Primer1	(Din)
8	Primer0	Primer0	(!Din)
9	Primer1	Segundo1	(Din)
10	Primer1	Primer0	(!Din)
11	Quinto1	Sexto1	(Din)
12	Quinto1	Primer0	(!Din)
13	Segundo1	Tercer1	(Din)
14	Segundo1	Primer0	(!Din)
15	Sexto1	Inicio	(!Din)
16	Sexto1	eReset	(Din)
17	Tercer1	Primer0	(!Din)
18	Tercer1	Cuarto1	(Din)

	Name	Inicio	Sexto1	Quinto1	Cuarto1	Tercer1	Segundo1	Primer1	Primer0	eReset
1	eReset	0	0	0	0	0	0	0	0	0
2	Primer0	0	0	0	0	0	0	0	1	1
3	Primer1	0	0	0	0	0	0	1	0	1
4	Segundo1	0	0	0	0	0	1	0	0	1
5	Tercer1	0	0	0	0	1	0	0	0	1
6	Cuarto1	0	0	0	1	0	0	0	0	1
7	Quinto1	0	0	1	0	0	0	0	0	1
8	Sexto1	0	1	0	0	0	0	0	0	1
9	Inicio	1	0	0	0	0	0	0	0	1

Elementos lógicos: 8

 

b-

Copio solo la descripción de hardware que se incluyó a la descripción anterior.


```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;


entity hdlc_b is
port (clk, reset, Din: in std_logic;
      F: out std_logic
);
end hdlc_b;

architecture estructura of hdlc_b is
    type e is (eReset, Primer0, Primer1, Segundol, Tercer1, Cuartol, Quintol, Sextol, Inicio);
    signal estado:e;
    attribute enum_encoding : string;
    attribute enum_encoding of e : type is "0000 0001 0010 0011 0100 0101 0110 0111 1000";
begin
    process(clk, reset)
    begin
        if reset ='0' then
            estado<=eReset;
        elsif (rising_edge(clk)) then
            case estado is

```

 

Elementos lógicos: 5

 


C-

```


entity hdlc_c is
port (clk, reset, Din: in std_logic;
      F: out std_logic
);
end hdlc_c;

architecture estructura of hdlc_c is
    type e is (eReset, Primer0, Primer1, Segundol, Tercerl, Cuartol, Quintol, Sextol, Inicio);
    signal estado:e;
    attribute enum_encoding : string;
    attribute enum_encoding of e : type is "0000 0001 0011 0010 0110 0111 0101 0100 1100";
begin
    process(clk, reset)
    begin
        if reset = '0' then
            estado<=eReset;
        end if;
    end process;
end estructura;

```

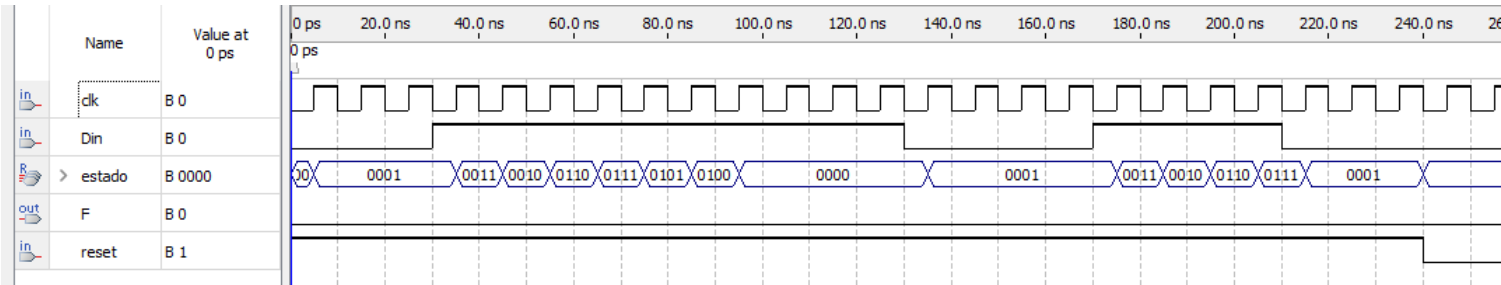

Elementos lógicos: 8

 

d-

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;

entity hdlc_d is
port (clk, reset, Din: in std_logic;
      F: out std_logic
);
end hdlc_d;


architecture estructura of hdlc_d is

    --type e is (eReset, Primer0, Primer1, Segundol, Tercerl, Cuartol, Quintol, Sextol, Inicio);


    attribute enum_encoding : string;
    subtype e is unsigned (3 downto 0);
    constant eReset : e := "0000";
    constant Primer0 : e := "0001";
    constant Primer1 : e := "0010";
    constant Segundol : e := "0011";
    constant Tercerl : e := "0100";
    constant Cuartol : e := "0101";
    constant Quintol : e := "0110";
    constant Sextol : e := "0111";
    constant Inicio : e := "1000";
    signal estado:e;

begin

    process(clk, reset)
    begin
```

 

Elementos lógicos: 8

 

e-

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;

entity hdlc_e is
port (clk, reset, Din: in std_logic;
      F, mensaje: out std_logic);
end hdlc_e;

architecture estructura of hdlc_e is

    --type e is (eReset, Primer0, Primer1, Segundol, Tercer1, Cuartol, Quintol, Sextol, Inicio);

    attribute enum_encoding : string;
    subtype e is unsigned (3 downto 0);
    constant eReset : e := "0000";
    constant Primer0 : e := "0001";
    constant Primer1 : e := "0010";
    constant Segundol : e := "0011";
    constant Tercer1 : e := "0100";
    constant Cuartol : e := "0101";
    constant Quintol : e := "0110";
    constant Sextol : e := "0111";
    constant Inicio : e := "1000";
    signal estado:e;

begin

    process(clk, reset)
    begin

        if reset = '0' then
            estado<=eReset;

        elsif (rising_edge(clk)) then
            case estado is

                when eReset => if Din='0' then
                                estado<=Primer0;
                            else
                                estado<=eReset;
                            end if;

                when Primer0 => if Din='1' then
                                estado<=Primer1;
                            else
                                estado<=Primer0;
                            end if;

                when Primer1 => if Din='1' then
                                estado<=Segundol;
                            else
                                estado<=Primer0;
                            end if;

                when Segundol => if Din='1' then
                                estado<=Tercer1;
                            else
                                estado<=Primer0;
                            end if;

                when Tercer1 => if Din='1' then
                                estado<=Cuartol;
                            else
                                estado<=Primer0;
                            end if;

                when Cuartol => if Din='1' then
                                estado<=Quintol;
                            else
                                estado<=Primer0;
                            end if;

                when Quintol => if Din='1' then
                                estado<=Sextol;
                            else
                                estado<=Primer0;
                            end if;
            end case;
        end if;
    end process;
end

```

```

when Sextol => if Din='1' then
    estado<=eReset;
else
    estado<=Inicio;
end if;

when Inicio => if Din='1' then
    estado<=eReset;
else
    estado<=Primer0;
end if;

when others => null;

end case;
end if;
end process;

process (estado)

begin

    if estado=Inicio then
        F<='1';
    else
        F<='0';
    end if;

end process;

```

```

process (clk, reset)

variable vector_guardado: std_logic_vector (7 downto 0);
variable i: integer;

begin

    if reset ='1' then
        if (rising_edge(clk)) then
            if Din='0' then
                vector_guardado(i):='0';
                i:=i+1;
            else
                vector_guardado(i):='1';
                i:=i+1;
            end if;
            if i=7 then
                i:=0;
            end if;
        end if;
    end if;

    if vector_guardado="01111110" then
        mensaje<='1';
    else
        mensaje<='0';
    end if;

end process;

end estructura;

```

